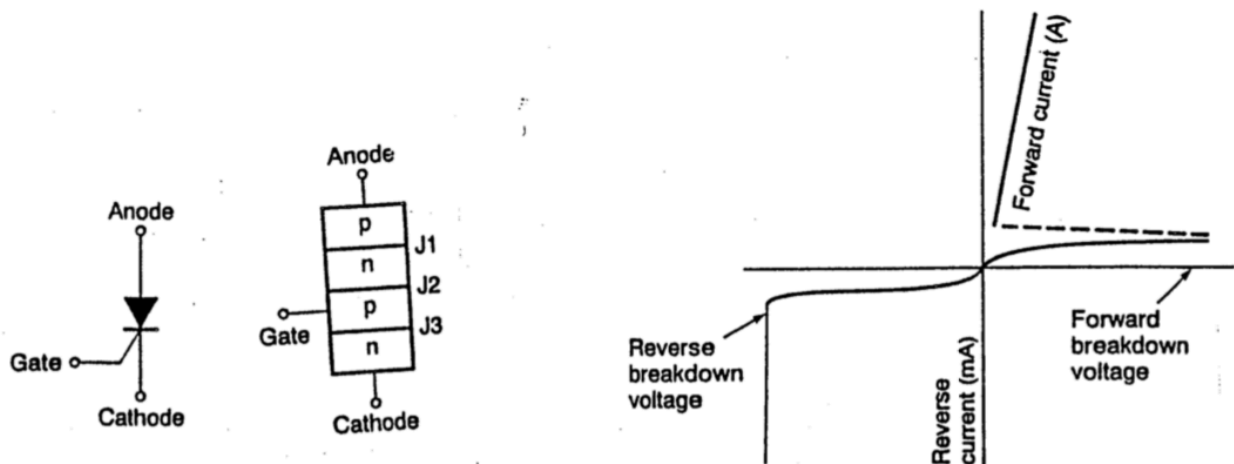


### Silicon Controlled Rectifier (SCR / Thyristor)

A thyristor is a high speed switch that can handle up to 1000A



#### When gate current OFF


- If anode is relatively positive to cathode, the thyristor is forward biased. Since the gate is OFF, the device is in forward blocking state.
- If anode is relatively negative to cathode, the thyristor is reverse biased. If voltage increase to a large value, the junction will break down and the thyristor is in conducting state with large current under negligible resistance.

#### When gate current ON (Gate current $\sim 10\text{mA}$ )

- The forward current blocking traits is gone, while the reverse blocking traits remain.
- Anode current (Load current) can pass through and is controlled by external impedance.
- $\sim 1\text{V}$  drop across the thyristor.
- Load current must  $>$  Latching current ( $I_L$ ), the thyristor will revert to blocking state (thyristor will turn off) if the load current  $<$  holding current ( $I_H$ ).
- **What happen between  $I_H$  and  $I_L$ ???**

Therefore, once the thyristor is triggered, there is no control except turning the load current  $< I_H$ .


Thyristor Operation Principle

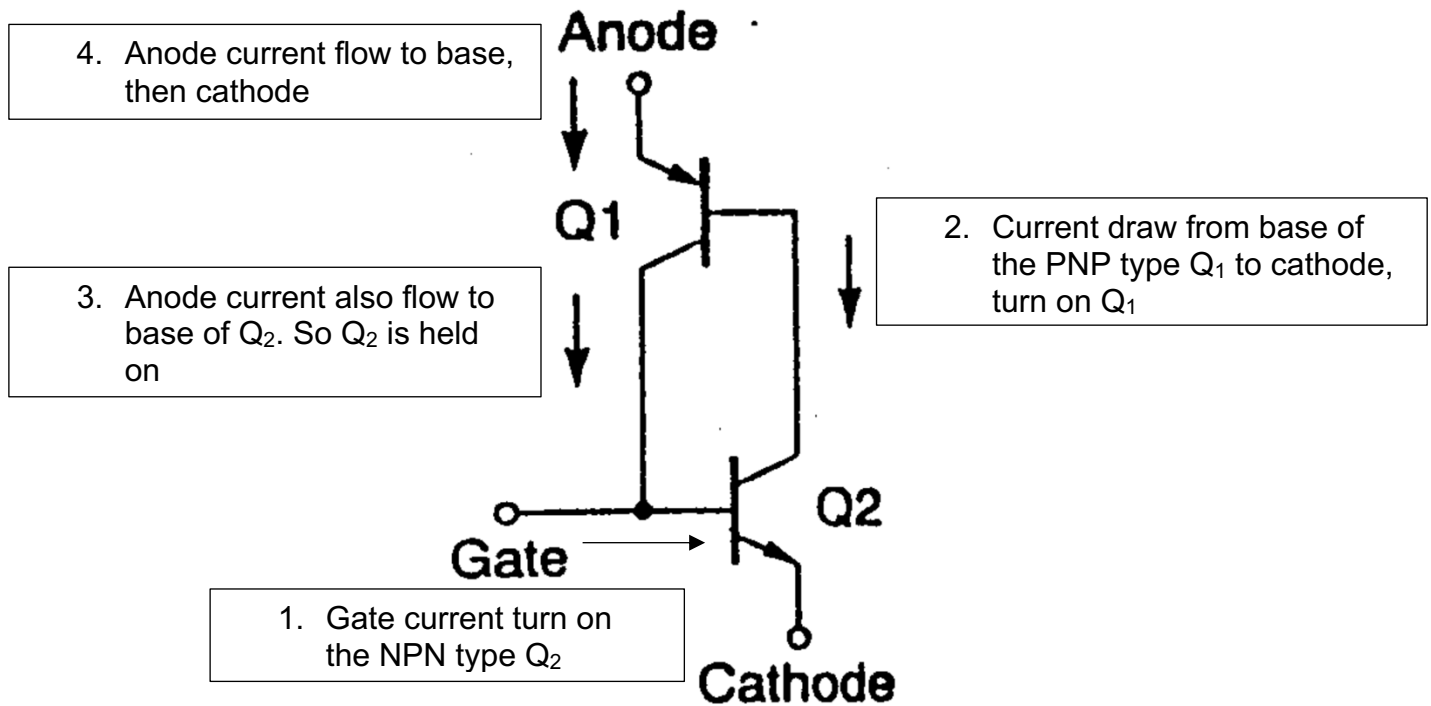


Therefore, once the gate is pulsed on, the SCR maintains its own gate current to lock the anode current

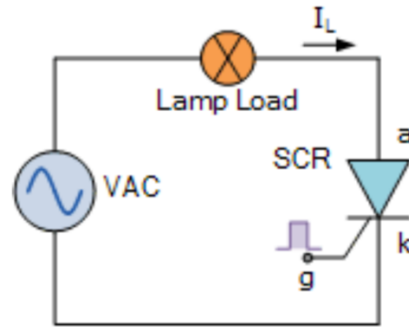**Thyristor controlled rectifier**

When a thyristor connected as shown is supplied by a sinusoidal voltage and is triggered at an instant corresponding to an angle  $\phi$ :



Waveforms:

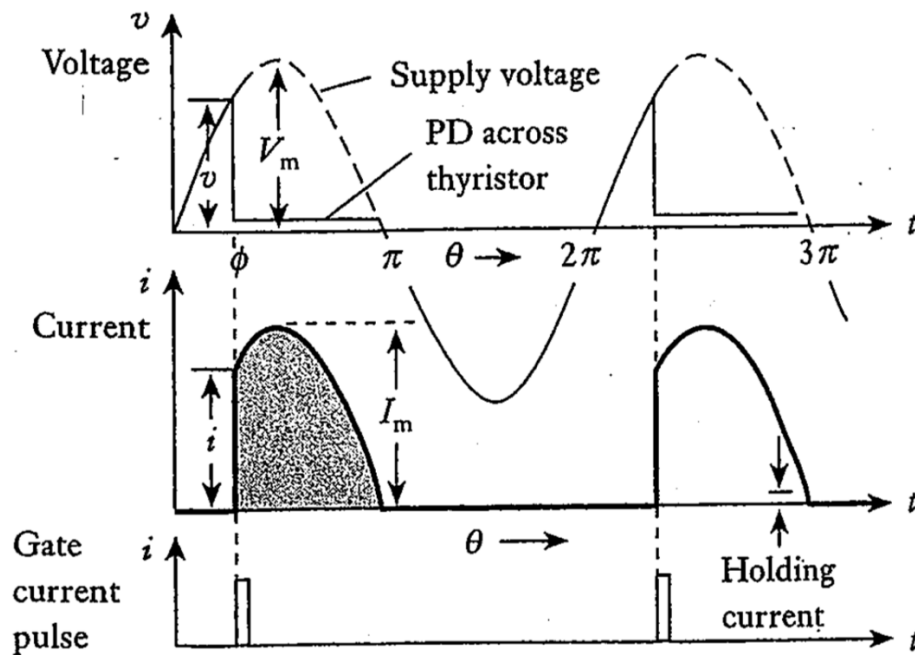

The average current is (by Mean Value Theorem):

$$\begin{aligned}
 I_{avg} &= \frac{1}{2\pi - 0} \int_0^{2\pi} I_m \sin(t) dt \\
 &= \frac{1}{2\pi} \left[ \int_0^{\phi} I_m \sin(t) dt + \int_{\phi}^{\pi} I_m \sin(t) dt + \int_{\pi}^{2\pi} I_m \sin(t) dt \right] \\
 &= \frac{1}{2\pi} \int_{\phi}^{\pi} I_m \sin(t) dt \\
 &= \frac{I_m}{2\pi} (1 + \cos\phi)
 \end{aligned}$$

For fully controlled rectifier, the average current will be:

$$I_{avg} = \frac{I_m}{\pi} (1 + \cos\phi)$$

For  $I_m$ , If  $V$  is AC:

$$\begin{aligned}V_m &= I_m R \\V\sqrt{2} &= I_m R\end{aligned}$$

Definition of Instantaneous Power (AC)

$$\begin{aligned}P_{inst} &= V(t)I(t) \\&= I(t)^2 R \\&= \frac{V(t)^2}{R}\end{aligned}$$


Definition of Average Power (AC)

$$P_{avg} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} P_{inst} dt$$

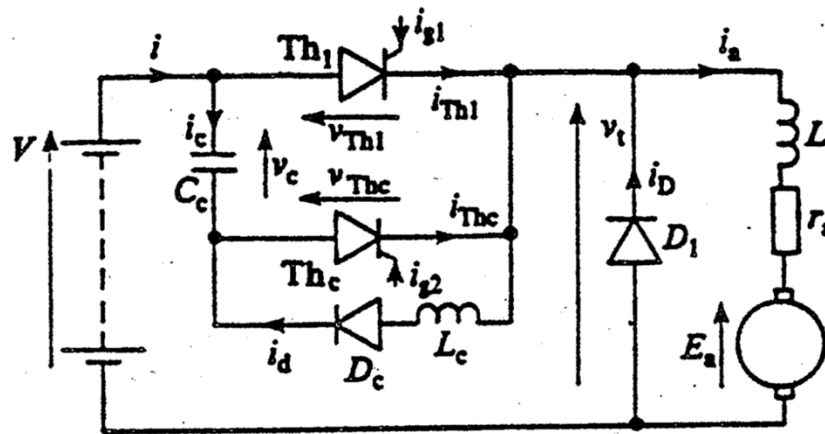**DC / DC Chopper**

A device that can control the input D.C. voltage by varying the on and off time of a converter.

This chopper circuit provides a variable armature current  $I_a$  for torque pulsations and subsequently, speed perturbations (擾動) about a mean value, which cause rotor acceleration and deceleration. The full circuit is:




The operation details are as follows:


At time  $t = t_{ON}$ :

1.  $Th_1$  receive an impulse  $i_{g1}$ , become forward biased. Supplying the armature with the voltage source  $V$

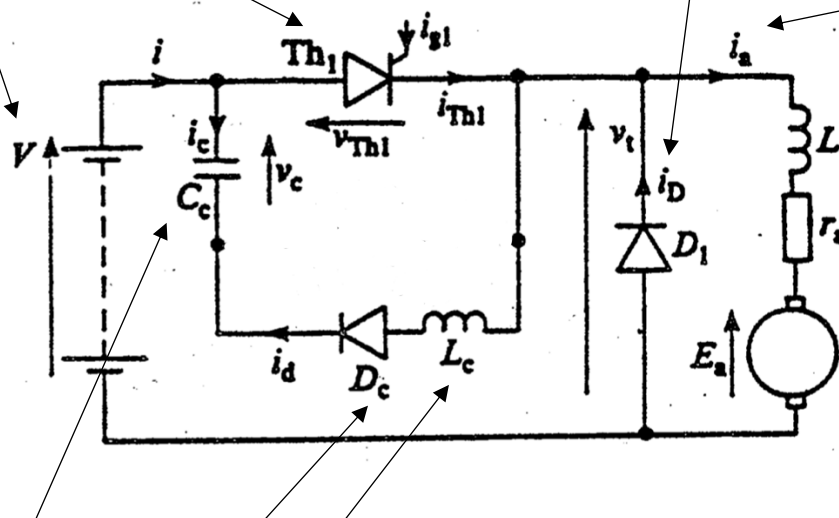2.  $i_a$  then increase exponentially, while  $i_D$  plunge to 0, because  $D_1$  is now reverse biased



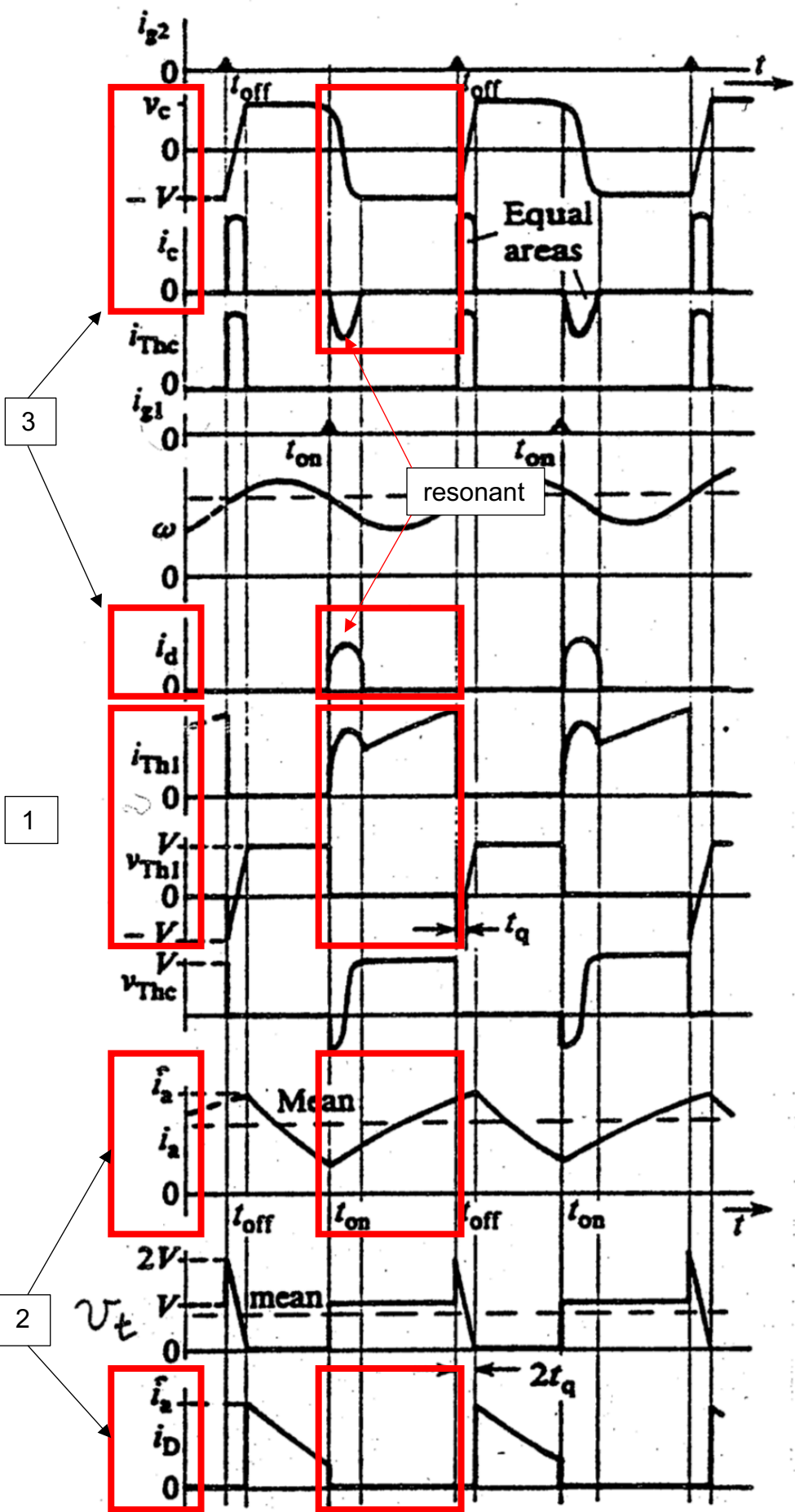3. Current also pass through this path, and  $C_c$  resonant (oscillate) for half a period with  $L_c$  with relation  $i_d = -i_c$  as  $v_c$  falls to 0. Energy transfer between them during oscillation and  $v_c = -V$  when the oscillation is finished. The diode  $D_c$  here prevent further oscillatory interchange.



At time  $t = t_{OFF}$ :


2. Since, for now,  $i_c = i_a = i$ ,  $Th_1$  has no current, so turned off

4. When  $v_c = V$ , the current  $i_a$  given by  $C_c$  will cease. The exponentially decreasing current  $i_a$  will then flow through the diode  $D_1$  such that  $i_D = i_a$ . At this point  $v_t = V - v_c \leq 0$ , and  $v_c$  maintain constant.

3. The capacitor  $C_c$  then have its voltage  $v_c$  increase at a fairly constant rate from  $-V$  to  $V$


1.  $Th_c$  received an impulse  $i_{g2}$ ,  $C_c$  will therefore discharge, such that  $i_c = i_{THC} = i_a$

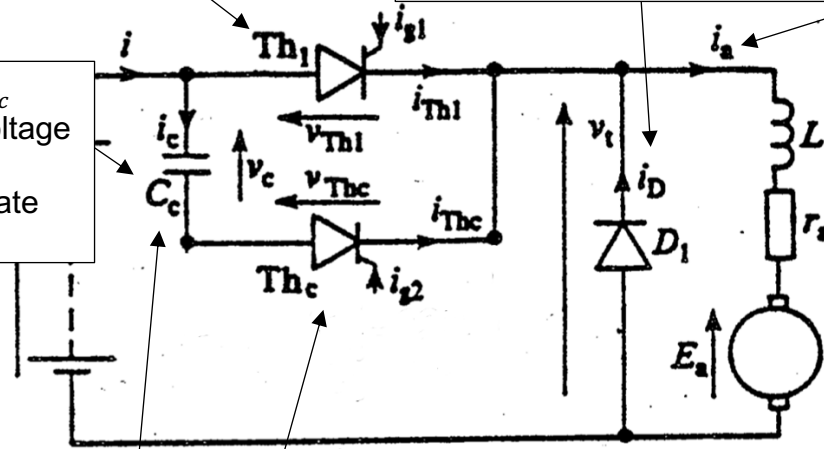5. The constant  $v_c = V$  and the exponentially decreasing current  $i_D = i_a$  are maintained until the time  $t = t_{ON}$



All in all:

- $Th_1$  is the main switching thyristor.
- $Th_c$  is the commutating thyristor to connect the capacitor  $C_c$  across the anode and cathode of  $Th_1$  to turn it off and maintaining negative anode cathode voltage for sufficient time to ensure recovery to the blocking condition.
- The armature inductance  $L$  is crucial to effective operation of the circuit because it provides a reservoir of energy and enable the armature current to be continuous, whereas the D.C. supply current  $i_{TH1} + i_c$  is pulsed.
- $D_1$  is the free wheel diode, which permits the armature current to be sustained by the stored energy of series inductance  $L$  to circulate and continue the development of torque.
- $D_c$  and  $L_c$  form a series resonant circuit with  $C_c$ , oscillate for a period of  $\frac{T}{2}$  only after  $Th_1$  has been triggered, thus reversing the polarity of  $C_c$ .

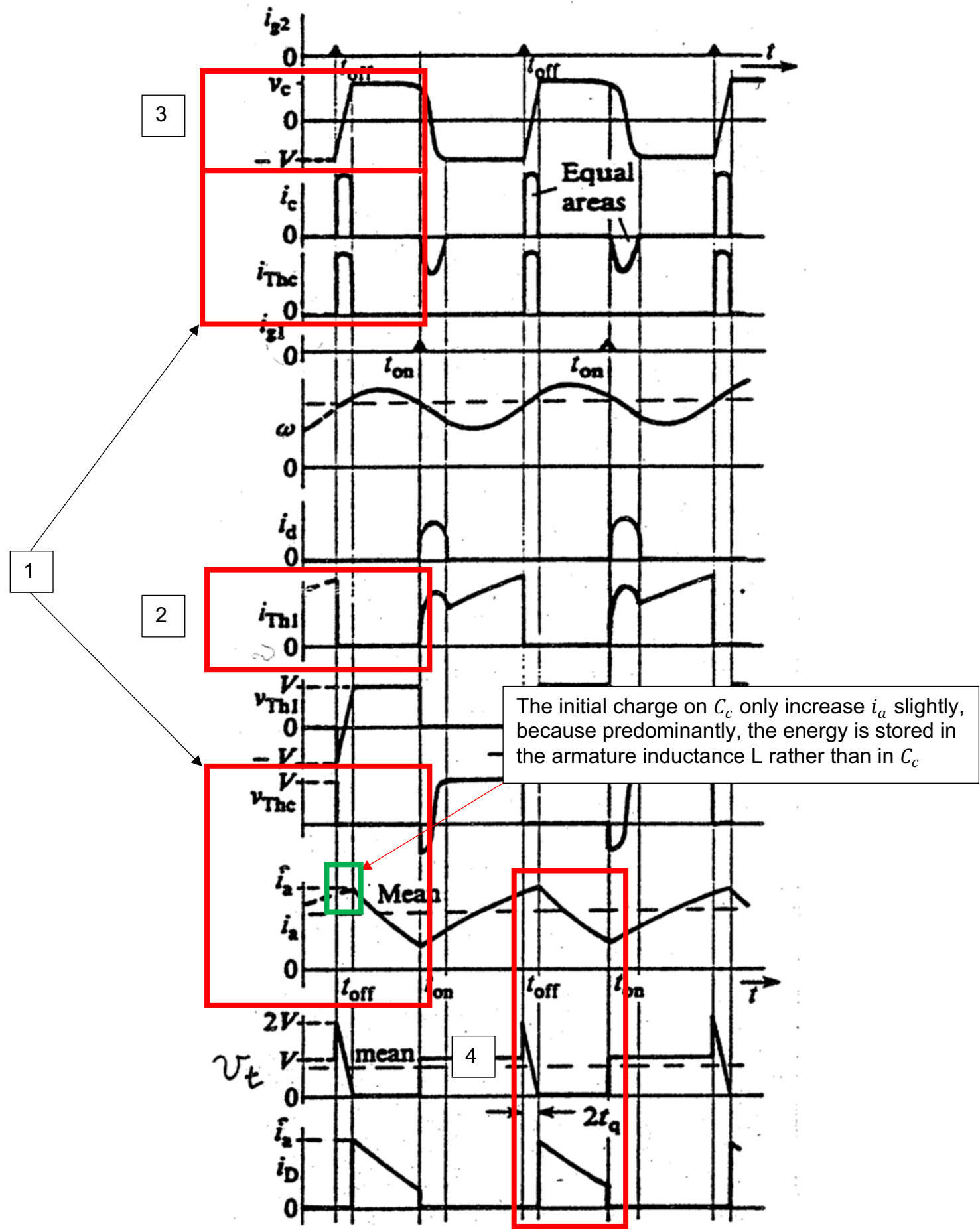





### Voltage and Current break down

[\*\* $t_{ON}$  is triggered at  $Th_1$ ,  $t_{OFF}$  is triggered at  $Th_c$ ]


Armature:

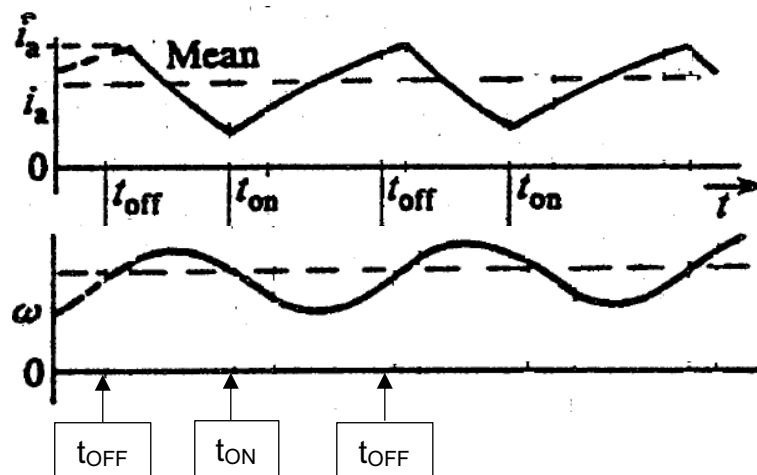


$Th_1$ :

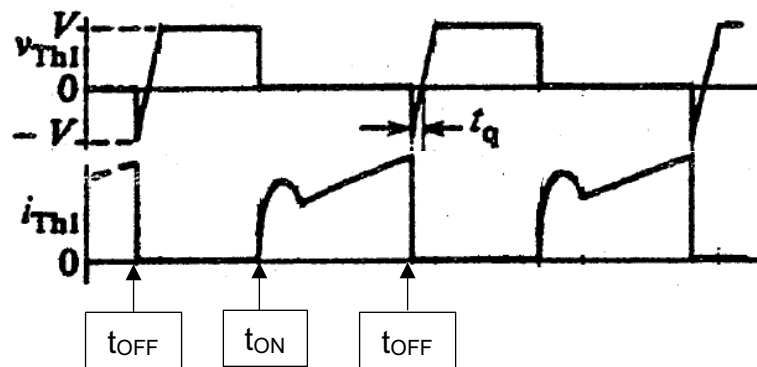


Capacitor:

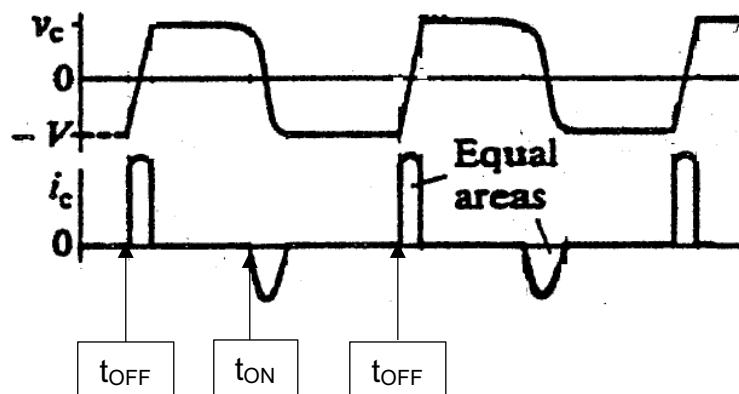


D<sub>c</sub>:

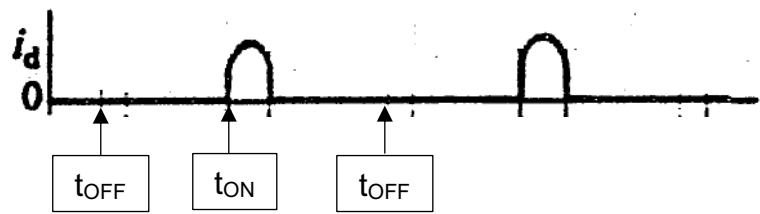

Th<sub>c</sub>:

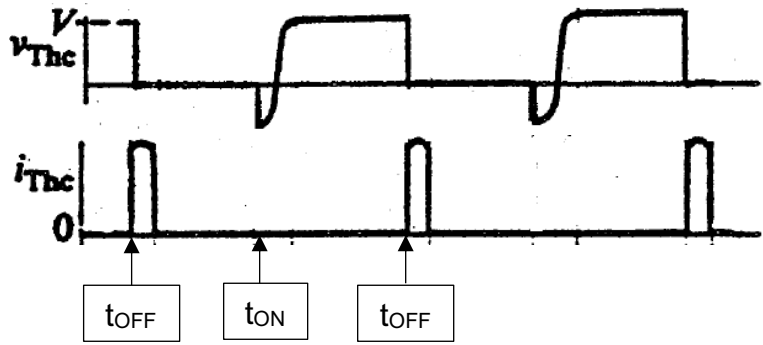


D<sub>1</sub>:

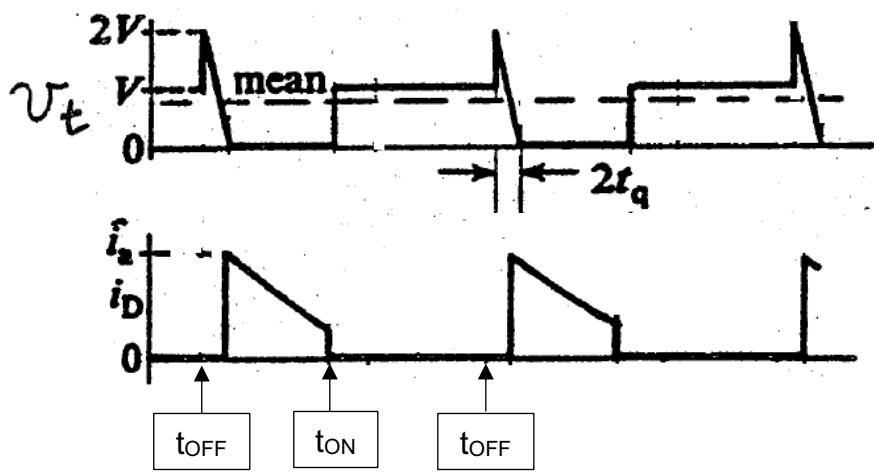

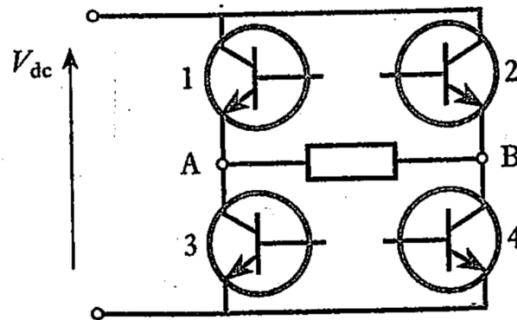**DC / AC inverter**

Such circuit is to change a waveform from D.C.  $\rightarrow$  A.C. The significance of this inversion process is that we can choose the frequency of the alternating signal, which is important when controlling the speed of an induction motor.

Circuit diagram of a one phase inverter circuit:




The D.C. supply can come from battery or rectified A.C. supply.



There are 2 ways to control the output voltage:

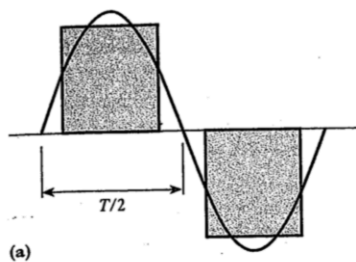1. Vary the input D.C. voltage, which require a controlled A.C. to D.C. converter. The converter needs extra cost and therefore usually used for high power applications.
2. D.C. input is derived from simple rectifier system. Pulse Width Modulation (PWM) is used to control the output voltage. This is cheaper and is used for lower power applications.

Below is a comparison of simplistic control and PWM control:



“Simplistic” control

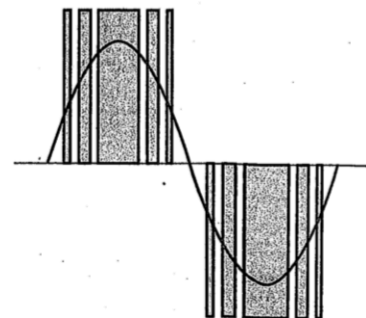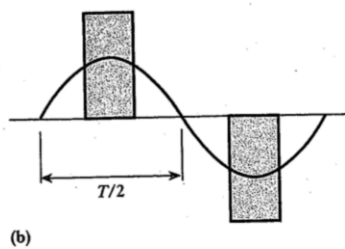

PWM control

### **Switching devices in inverters**

There are 4 types of switching devices:

- Bipolar Junction Transistors (BJT)
  - Can be switched off by simply switch off the base emitter current
  - Do not require a commutation circuit
  - Used in applications up to ~5kW with voltages up to 415 / 240V
  - Dissipate ~1% of the output power
- MOSFET
  - Can be easily turn on and off
  - Control circuit is less complex compared to BJT's, therefore cheaper
  - Power dissipation is higher than that of BJT's
- Insulated gate bipolar transistor (IGBT)
  - Gate can switch on and off easily
  - Power dissipation in the collector-emitter circuit is low
  - Power rating ~1MW with voltage rating ~1kV
  - Brings together the advantages of BJT and MOSFET
- Gate turn off thyristor (GTO)
  - Can be switched off by a negative gate-cathode current, unlike conventional thyristor
  - Usually deal with high power ratings, around a few MW
  - Require higher gate pulses
  - Double forward voltage drops compare with the conventional ones